

Hello students.

I am Cajé Francis Pinto, Assistant Professor from
Department of Electronics at St. Xaviers College
Mapusa Goa.

Today we'll be doing Unit 3: Signal Conditioning and the
module name is basics of instrumentation amplifier,
instrumentation system. The module number is 19.

The outline of the module is Instrumentation amplifier,
Schematic of an instrumentation amplifier,
an Instrumentation system.

Through this module, the students will be able to explain the
working of an instrumentation amplifier, Design and construct
an instrumentation system.

Let us begin with our module.

An instrumentation amplifier amplifies low level signal
output of an electrical transducers before any further
processing. So when you have to select an instrumentation
amplifiers, there are important features. The first
one: Selectable gain with high gain accuracy and high gain
linearity. Differential input capability with high gain
common mode rejection.

3rd: High stability of gain with low temperature coefficient.

4th: Load DC offset and drift errors, which is referred to the input. And finally low output impedance.

So the diagram what you see over here is the circuit for an instrumentation op amp. So

basically you require three op amps.

So over here we have A1 and A2 which is called as the input buffer and it has a unity gain for common mode signals.

And the gain is $1 + 2 \text{ times the value of } R2 / R1$ for differential signals.

Now $E1 + E_{cm}$ is the voltage applied to the A1 amplifier. $E2 + E_{cm}$ is the input voltage applied to the A2 amplifier.

Now this particular opamp A3 is called as a difference amplifier and the gain is chosen in such a way depending on the values of $R4$ $R5$ $R6$ and $R7$.

We shall look into details.

So let us assume that the value of $R4$ $R5$ $R6$ and $R7$ are the same.

So now we need to know what is the voltage at $E3$ and what is the voltage at $E4$.

So over here, if you want to know what is the voltage at $E3$,

It is because of two reasons: it is because of the voltage E_1 and E_{cm} and also because of the voltage of E_2 plus E_{cm} .

So over here, the first thing

is If you look at this particular op amp A1 it is a

non inverting amplifier and A2 also is a non inverting

amplifier. The gain of a noninverting amplifier is given as

A_v is equal to $1 + R_F$ upon R_1 . So R_F is your feedback

resistor, so in this case R_2 is your feedback resistor

for A1 and R_3 is your feedback resistor for A2.

And your input resistor will be

R_1 . Now, If it was a inverting amplifier, the gain of

inverting amplifiers given as A_v is equal to minus R_F upon R_1

, so therefore your voltage at E_3 will be equal to $1 +$

R_2 divided by R_1 multiplied by the input voltage i.e E_1 .

Minus R_2

upon R_1 into E_{cm} plus E_2 . now why this voltage is

occurring in this particular equation is because.

When this particular voltages is there due to virtual ground, the

same potential is there across the inverting terminal and

therefore this voltage is also applied through R_1 . So

similarly the voltage at E_4 will be written as E_4 is equal to 1

+ R_3 divided by R_1 multiplied by E_2 . This is

because of the voltage applied to the second of op amp minus

R_3 upon R_1 into E_{cm} plus

E_1 . E_{cm} is the common mode voltage, so it can be noise or

it can be at any common voltage which is present at both

the inputs. So finally

if the value of R_2 and R_3 are the same and it is very very

important that the values of R_2 and R_3 are the same.

You take the difference of E_4 and E_3 . So E_4 , when you take

subtraction of E_4 and E_3 , the output voltage will be given as

$1 + 2$ times the value of R_2 divided by R_1 into E_2 minus E_1 .

So after solving this. i.e $E_4 - E_3$ there are some

terms will be cancel out i.e. E_{cm} and E_{cm} will be cancelled out and

other terms will be

Added, so this particular voltage, that is E_0 will be

produced if and only if the values of R_4 R_5 R_6 and R_7 are the same.

It is called as unity differential amplifier. But if

The values of R_4 and R_5 are different, that is ill take an

example if R_4 and R_6 are the same like for 1K ohm and R_5 and

R_7 is the same 10 K ohm. Keep this in mind the gain is

10. So whatever is the difference between E_4 minus E_3

this voltage will be amplified 10 times at the output. So the gain of the instrumentation amplifier can be varied by just changing the value of R1, so this entire construction. What you have seen over here, it consists of three op amps. The 1st two op amps are called as a unity buffer opamp. The Third Opamp is called as a differential amplifier, so you can use OP 07 or you can use 741 IC to construct an instrumentation op amp, so this is what is present in an Instrumentation op amp

Now coming up, the next topic is an instrumentation system.

The measurement and control of physical condition is very important in many industrial and consumer applications.

It is very important to measure the output signal produced by the transducer and also it is mere important to control the physical condition by producing the output signal.

An automatic process controller is used at the output stage to compensate for the changes in the operating condition.

Now this is the block diagram of the instrumentation system. It consists of three stages. The first stage is called as the input stage.

The second stage is called as the intermediate stage and the third one is called as the output stage, which is having

output amplifier. So the physical quantity to be measured is going to be sensed by your input stage, which is consisting of a transducer and preamplifier. So a transducer will convert the physical quantity into an electrical form. It can be in terms of current or it can be in the form of voltage. So this particular signal is supplied to the intermediate stage. So what you see over here is a transmission lines. So whenever input stage is connected to the intermediate stage, you need transmission wires to transfer signal for one point to the other point. The Function of the intermediate stages it requires to amplify the low level Signals, now why do we need to amplify low level signals because in order to produce an output you need to produce it on the indicating device. It can be on a meter or it can be on a digital display. So the signal has to be modified so that it can be displayed on the output.

Now, This entire thing What Have you seen is very very Important in making an instrumentation system.

These are my references and with this we come to the end of the module. Thank you.