

Hello students.

I'm Cajé Francis Pinto.

Assistant Professor from Department of Electronics at

St. Xavier's College, Mapusa,

Goa. Today we'll be covering Unit 3 signal conditioning and

the module name is instrumentation amplifier using

Transducer bridge, an chopped and modulated DC amplifier.

The model number is 20.

The outline of this module is instrumentation amplifier using

transducer bridge. And chopped modulated DC amplifier.

Through this model, the student will be able to

explain the working principle of

instrumentation amplifier using a transducer bridge

and explain the working principle of a chopped and

modulated DC amplifier.

Let us begin with the module.

So in the previous lecture we learned about instrumentation

amplifier. Now over here.

The instrumentation amplifier is connected to a transducer

bridge. The resistive transducer is connected to one arm of the

bridge, so you can use a resistance thermometer. You can

use a strain gauge or any other

resistive transducer. R_T is the resistance of the

transducer, and ΔR is the change in resistance of

the resistive transducer.

The values of our R_A , R_B and R_C are chosen in such a way

that it is almost equal to the values of R_T .

The total resistance of the transducer is given

as R_T plus ΔR .

The condition for the bridge to be balanced V_B has to be equal

to V_A or.

R_B divided by total resistance that is R_B plus R_C into E

should be equal to R_A divided by total resistance. That is R_T

plus ΔR into E , so we're using over here. A simple method called

as voltage divider method.

In simple words, the ratio of R_B upon R_C has to be equal to R_A

upon R_T , so this is a very important thing required in

order to balance the.

Bridge.

Now the bridge will be balanced for the desired reference

conditions, so depending on what temperature you want the bridge

to be balanced, you can balance the bridge. So as the physical

quantity changes, the resistance of the transistor also changes, causing the bridge to be unbalanced and the output voltage what is produced at the.

3rd Opamp is the function of the change and resistance of the transducer.

Let us go into detail.

The potential at V_B will always be constant, but potential at V_A will always be varying depending on the change in resistance. So the value of V_B is given as R_B divided by total resistance.

That is R_B plus R_C into E is your voltage required for exciting the Wheatstone bridge.

V_A is given by R_A divided by total resistance that is R_A plus R_T plus Δ into E . So when the bridge is balanced the potential of V_A & V_B will be the same. But if there's any change in physical quantity, the potential of V_A will vary. So

keep this in mind. The potential of V_A is applied to the 1st.

Input of the opamp that is A_1 and potential V_B is applied to the input of the second of opamp.

Both opamps A_1 and A_2 act as a unity buffer amplifier.

Normally a buffer is used to provide you high input impedance and low output impedance.

And the third. Amplifier is used as a differential amplifier, so

if the values of all these four are the same, this particular

becomes a subtractor.

So the gain of this particular amplifier is 1, but in this

particular example we have made the values of R_1 and R_2 the same

and the values of R_3 and R_F the same. This V_{AB} will be amplified

with the gain of R_F upon R_1 .

So this is how you can construct a instrumentation

amplifier to measure.

Temperature to measure intensity of light or to measure any other

physical condition which refers to resistive transducer.

So the applications of instrumentation amplifier is.

You can make the entire.

Circuit as a temperature indicator using thermistor

you can make a light intensity meter or you can

also use as a analog weight scale.

Now coming to the next topic will be doing chopped and modulated

DC amplifier.

A chopper amplifier is an amplifier where the DC input

voltage is literally chopped to produce an AC signal.

This signal is amplified by a standard AC amplifier and

finally it is converted back to a DC signal.

The chopping action can be in two ways, electronical or mechanical, so this is just clear glimpse of how does a chopper modulated DC amplifier looks. Initially we have a DC input, the DC input is going to be converted into an AC input.

These AC input will be amplified by an AC amplifier, called as AC output, and finally it will be converted back to your DC output. So if you have notice, the level of your DC input has been. Increased

now coming to the explanation of a chopped Modulated DC amplifier.

It consists of two Transformers.

Input Transformer and output transformer. V_i is the input DC voltage. So this switches alternately connects between

A & B. Keep this in mind. Also there's another switch which is connected at the output. Both the switches are gang tuned,

meaning that connected together. So when this is connected on the top point it is a. This also is

connected on Top point, when the switch is coming down to

B this also switches connected towards the bottom

point so when switches at position A the current flows in

One Direction. But when the switch is connected to position

B, the current flows in the

opposite direction. Therefore, a AC voltage will be induced in the secondary winding.

The peak value of the induced voltage is proportional to the value of your DC input. So Suppose the input voltage 10 millivolts. The peak voltage also will be 10 millivolts, and the negative peak also will be 10 millivolts.

Now this induced voltage what is produce will be amplified by a simplifier. An amplified square wave appears at the primary winding at the output of the transformer. Now this AC signal will be converted back to the DC signal.

The secondary winding of the output transformer is centrally taped with an output switch which is mechanically coupled to the input switch.

This is the waveforms of.

A chopped and more later DC amplifier. This is the input voltage across the primary winding of the output transformer and this is the output voltage of the secondary winding of the output transformer. With this we have completed our module in chopped and modulated DC amplifier.

These are my references.

Thank you.