

1. Draw the circuit diagram and obtain balance conditions for Hay's bridge.
2. Compare Maxwell's bridge and Hay's bridge.
3. Explain with a diagram how Schering's bridge can be used to measure unknown capacitance.
4. Draw the circuit diagram and obtain balance conditions for Schering's bridge.