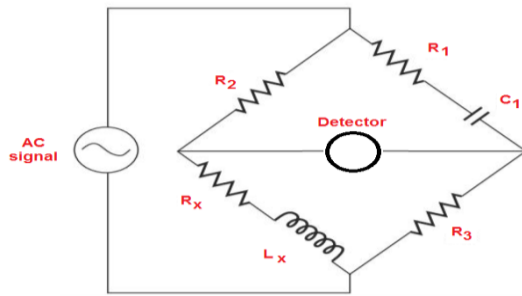


Hay bridge



$$R_x = \frac{R_2 R_3}{R_1 [1 + Q^2]}$$

$$L_x = \frac{C_1 R_2 R_3}{[1 + \frac{1}{Q^2}]}$$

$$Q = \frac{1}{\omega C_1 R_1}$$

The Hay bridge differs from Maxwell's bridge by having a resistance R_1 in series with a standard capacitor C_1 instead of a parallel. The term ω appears in the expression for both L_x and R_x , which indicates that the bridge is frequency sensitive.

- Used for inductance measurements of high Q (>10).
- Measure from 1 μH to 1000 H with an accuracy of $\pm 2\%$.
-

At balance $Z_1 Z_x = Z_2 Z_3$, where

$$Z_1 = R_1 - j/\omega C_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_x = R_x + j\omega L_x$$

Substituting these values in the balance equation we get

$$\left(R_1 - \frac{j}{\omega C_1}\right)(R_x + j\omega L_x) = R_2 R_3$$

$$R_1 R_x + \frac{L_x}{C_1} - \frac{j R_x}{\omega C_1} + j\omega L_x R_1 = R_2 R_3$$

Equating the real and imaginary terms we have

$$R_1 R_x + \frac{L_x}{C_1} = R_2 R_3 \quad (1) \quad \text{and} \quad \frac{R_x}{\omega C_1} = \omega L_x R_1 \quad (2)$$

Solving for L_x and R_x we have, $R_x = \omega^2 L_x C_1 R_1$.

Substituting for R_x in Eq. (1)

$$R_1 (\omega^2 R_1 C_1 L_x) + \frac{L_x}{C_1} = R_2 R_3$$

$$\omega^2 R_1^2 C_1 L_x + \frac{L_x}{C_1} = R_2 R_3$$

Multiplying both sides by C_1 we get

$$\omega^2 R_1^2 C_1^2 L_x + L_x = R_2 R_3 C_1$$

$$L_x = \frac{R_2 R_3 C_1}{1 + \omega^2 R_1^2 C_1^2} \quad (3)$$


Substituting for L_x in Eq. (2)

$$R_x = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{1 + \omega^2 R_1^2 C_1^2} \quad (4)$$

The term ω appears in the expression for both L_x and R_x .

This indicates that the bridge is frequency sensitive.

SCHERING BRIDGE

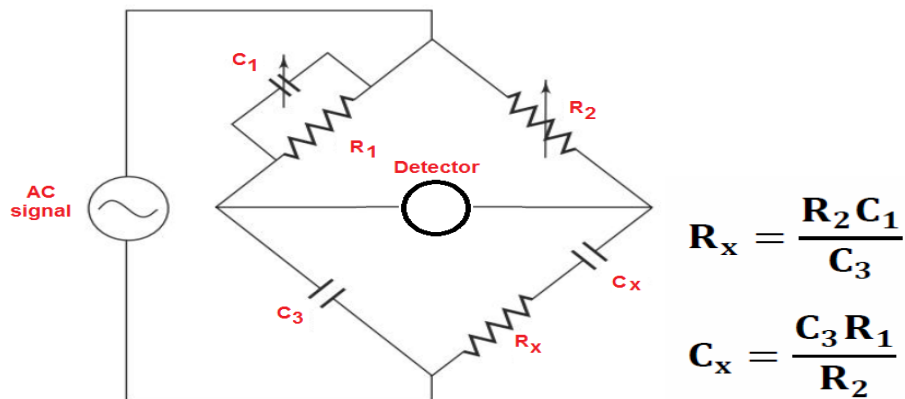

Used for the measurement of capacitors.

- Used for bridge measurements in the range of 100pF -1μF with accuracy of $\pm 0.2 \%$.

For balance, the general equation is

$$Z_1 Z_x = Z_2 Z_3 \quad (1)$$

$$Z_x = \frac{Z_2 Z_3}{Z_1}, Z_x = Z_2 Z_3 Y_1$$

$$Z_x = R_x - j/\omega C_x$$

$$Z_2 = R_2$$

$$Z_3 = -j/\omega C_3$$

$$Y_1 = 1/R_1 + j \omega C_1$$

$$Z_x = Z_2 Z_3 Y_1$$

$$\left(R_x - \frac{j}{\omega C_x} \right) = R_2 \left(\frac{-j}{\omega C_3} \right) \times \left(\frac{1}{R_1} + j \omega C_1 \right)$$

$$\left(R_x - \frac{j}{\omega C_x} \right) = \frac{R_2 (-j)}{R_1 (\omega C_3)} + \frac{R_2 C_1}{C_3}$$

Equating the real and imaginary terms, we get

$$R_x = \frac{R_2 C_1}{C_3} \quad (2) \quad C_x = \frac{R_1}{R_2} C_3 \quad (3)$$