

Quadrant -IV Assessment (Module-wise)

Programme :- S.Y. B.Sc.

Subject : Physics

Semester : III

Paper Code : PYC103

Paper Title : Waves and Oscillation & Electronics

UNIT II : Electronics

Module Name : UNIT 7: Linear IC's and Operational Amplifiers

Module Number : 29

Name of the presenter Shakeel alias AGA D. A.

Associate Professor

- 1) Draw the block diagram of IC 741 OP-AMP and explain.
- 2) Explain the characteristics of an OP-AMP.