

## **Quadrant II – Transcript and Related Materials**

**Programme: Bachelor of Science (Third Year)**

**Subject: Physics**

**Paper Code: PYC 106**

**Paper Title: ANALOG AND DIGITAL ELECTRONICS**

**Unit: 1 TRANSISTOR MULTIVIBRATORS**

**Module Name: Monostable Multivibrator**

**Name of the Presenter: Efrem D' Sa M.Phil, Ph.D.**

---

### **Transcript**

Unit 1 Transistor multivibrators,

Module name Monostable multivibrator

Module #3 Outline Working of monostable multivibrator using transistors.

Learning Outcomes

Understands the basics of monostable multivibrator.

Use of transistors in monostable multivibrator.

Apply monostable multivibrator's in electronics circuits.

The basic multivibrator configuration

consists of two inverting amplifiers, inverting amplifier 1 and inverting amplifier 2.

Inverting amplifier is coupled too inverting amplifier 2

through a coupling network N1

and inverting amplifier 2

is coupled through network N2 to

the input of inverting amplifier one

The nature of coupling networks

between two stages determine

the type of multivibrator.

This is a diagram of

transistor multivibrator.

The output of transistor one is

collector couple to the base

of transistor Q2 through a capacitor

C1 and the output of transistor Q1 (Q2)

is resistively coupled

through the base of transistor Q1.

This transistor multivibrator acts as

a monostable multivibrator.

This is the diagram of a monostable

multivibrator with the input

output waveforms of Monostable multivibrator,

Monostable multivibrator,

or one shot or monoshot,

or driven multivibrator,

It has only one stable state and one quasi stable state.

It remains in a stable state until an

input pulse triggers it into the other state.

that is a quasi stable state and

after time interval determined by the circuit constants,

the circuit remains ...returns to its initial stable condition,

where it remains until the next triggering pulse.

So a small triggering input

generates a large pulse.

The width of which is under the control of circuit designer.

Application of a positive going pulse to the base of transistor Q1 of

sufficient magnitude to make Q1 conduct appropriately lowers

the potential of VC1 to zero this forces the base of transistor

Q2 from zero to near minus VCC,

turning Q2 of immediately after this

instant capacitor C1 begins charging from

minus Vcc towards plus Vcc.

Through resistor R2.

However, as C1 begins to charge towards

plus Vcc, the voltage across C1  
is transmitted to the base of T2

And therefore as soon as the base of T2 becomes slightly positive, T2 turns on again so that the capacitor C1 does not have a chance to reach plus  $V_{cc}$  Volts. When Q2 conducts, its collector voltage goes to near 0 and the base of Q1 follows the change to a voltage below cut off. The trigger pulse is no longer being present. So the initial stable condition of T1 off and T2 on is restored,

The various waveforms are shown in Figure 2.

The pulse width  $T_w$  is determined by the time constant  $R_1C_1$

which controls the delay time

for Q2 in the off condition.

Expression for the width of the pulse.

We consider  $V_{B2}$  voltage at

base of transistor Q2

during discharge and is given by

the relation  $V_{cc} - i_{C1}R_1$  the

initial discharge current of

$i_{C1}$  is  $V_{CC}$  plus  $V_{CC} / R_1$ .  
 $i_{C1}$  is given by the relation

$2 V_{CC}$  divided by  $R_1$  into  $e$  raise to minus tau divided by  $R_1 C_1$ .

$V_{B2}$  is equal to  $V_{CC}$  minus  $2V_{CC} / R_1$

$e$  raise minus  $t$  divided by  $R_1 C_1$  into  $R_1$ .

We assume that  $Q_2$  switches on when  $V_{B2}$  is 0.

Substituting the value of the  $V_{B2}$  is equal to 0.

We get tau equal to  $R_1 C_1 \log 2$  which is equal to  $0.694 R_1 C_1$ .

Which is equal to the pulse width  $T_w$  which is equal to  $t$

By applying a separate voltage to the resistor  $R_1$ ,  $V_{BB}$  Base resistor  $R_1$

Pulse width  $T_w$  is given by relation

$R_1 C_1 \log \frac{1 + V_C}{V_{BB}}$

by changing the value of voltage  $V_{BB}$   
the pulse width can be changed and this gives rise

to a voltage to time converter.

The uses of monostable multivibrator.

It is used as a timer introducing time delay.

Small signal generates large pulse.

Reshaping ragged pulses, Changing the width of  
the pulse, stretch short input pulses

narrow wide pulses, blocking multiple

pulses into a single output pulse,  
generate gating signals, etc.

The notation used  
 $i_C$  for current

V for voltage, R for resistors,

C for capacitor, T capital T for period, t for time,

f for frequency.

$\tau$  for time constant, I slash P for input,  
or slash p for output.

I have referred to the following references,

Thank you.